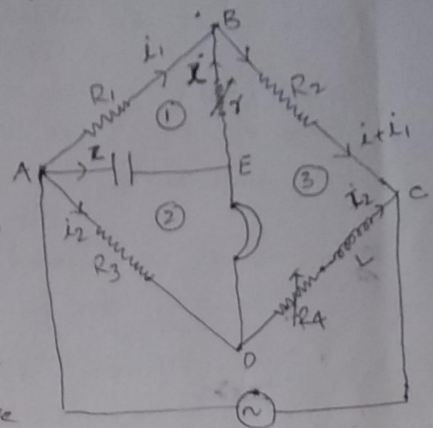


Q Describe the Anderson's bridge method for the measurement of the inductance of a coil. Draw the vector diagram of the balanced bridge.

Ans Anderson's bridge:-

This is the modified form of Maxwell's bridge which gives inductance L in terms of a fixed standard capacitor C . But here the imperfection of the capacitor has no effect on the measured value of L . So in this respect it is superior to Owen's bridge and it is the most preferred bridge for measuring L . Here the test coil L is placed in the fourth arm in series with a non inductive resistance R_4 . All other branches consists of non inductive



resistances. A non inductive variable resistance r is connected in series with the detector and the junction E of the detector with r is joined to A through the standard capacitor C . The balance condition is not given by the general balance condition of an a.c bridge. Suppose i be the instantaneous current through C from A to E , i_1 through R_1 from A to B and i_2 through R_3 from A to D . At balance there is no current through the head phone. The current through r is also i and through R_2 is $(i+i_1)$ by point rule, and that through L is i_2 .

Applying loop rule to loop ①

$$\frac{i}{j\omega C} + r i - i_1 R_1 = 0 \quad \text{or} \quad i_1 = \frac{i}{R_1} (r + \frac{1}{j\omega C}) \quad \text{--- ①}$$

Applying loop rule to loop ②

$$\frac{i}{j\omega C} - i_2 R_3 = 0 \quad \text{or} \quad i_2 = \frac{i}{j\omega C R_3} \quad \text{--- ②}$$

Applying loop rule to loop ③

$$i r + (i+i_1) R_2 - i_2 (R_4 + j\omega L) = 0 \quad \text{--- ③}$$

from ①, ② and ③ we have

$$i r + \left\{ i + \frac{i}{R_1} (r + \frac{1}{j\omega C}) \right\} R_2 - \frac{i}{j\omega C R_3} (R_4 + j\omega L) = 0$$

$$\text{or, } r + R_2 + \frac{R_2}{R_1} (r + \frac{1}{j\omega C}) - \frac{R_4}{j\omega C R_3} - \frac{L}{C R_3} = 0$$

$$\text{Equating real part to zero} \quad r + R_2 + \frac{R_2 r}{R_1} - \frac{L}{C R_3} = 0$$

$$\text{or, } L = CR_3 \left[\gamma \left(1 + \frac{R_2}{R_1} \right) + R_2 \right] \quad \text{--- (4)}$$

Equating imaginary part to zero $\frac{R_2}{R_1 \omega C} - \frac{R_4}{\omega C R_3} = 0$

$$\therefore \frac{R_1}{R_2} = \frac{R_3}{R_4} \quad \text{--- (5)}$$

The second balance condition is satisfied by adjusting R_4 and the first condition is satisfied by adjusting γ . Therefore by adjusting γ and putting the value of R_1, R_2, R_3 and C in eqⁿ (5) we may calculate self inductance L . From eqⁿ (4) & (5) it is also clear that the condition of the balance is independent from the source frequency.

For the condition of balance it is necessary that $L > CR_2 R_3$ otherwise γ will be negative. In the experiment we always take $R_1 = R_2$ \therefore for condition of balance $R_3 = R_4$. In this situation self inductance will be $L = CR_3(2\gamma + R_2)$.

The accurate value of L will be obtained only when the bridge is balanced sensitive. For the sensitivity of the bridge

$$C = \frac{L}{2R_4^2} \quad \text{or} \quad \frac{C}{L} = 2R_4^{-2}$$

Now taking $R_3 = R_4$ we get $\frac{L}{C} = 2R_3^2 = R_3(2\gamma + R_2)$

or $2R_3 = 2\gamma + R_2$ or $R_3 = \frac{2\gamma + R_2}{2} = \gamma + \frac{R_2}{2} = R_4$

Thus for the sensitivity and balance of the bridge R_4 and γ should be adjusted.

vector diagram of bridge:

Let AC represent the applied voltage. The current I_2 through branch ADC lags the applied voltage as it is inductive. So draw a line at A in the clockwise direction. This line gives the direction of I_2 . Cut off a length $AD = R_3 I_2$ to represent the voltage across R_3 . Draw $CO \perp$ from C on AO.

Then $CO = I_2 \omega L$ and $DO = I_2 R_4$

Since D and E are at the same potential E lies at the same position as D in the vector diagram. Therefore $AE = AD = \frac{I_1}{\omega C}$

$I_1 = \dots$ r.m.s value of current in ABC

$I_2 = \dots$ r.m.s value of current in ADC

Since current leads the voltage in a capacitor, the current I is \perp to AE in a anticlockwise direction. Cut off a length $EB = \gamma I$ along I to represent the voltage across γ . Join B with C and A. Then AB is the direction of I_1 and $AB = I_1 R_1$ and $BC = (I + I_1) R_2$.

